

# CMPU-224 Lab8 Quiz

## Spring 2025

Name: \_\_\_\_\_

This is a closed book, closed notes quiz. No electronic devices are allowed. You have until 3:30pm to complete the quiz. There are a total of 4 questions and 10 points.

There should be enough space on the quiz for your answers. If you need more space to work out a problem, blank paper will be available, just ask.

If you finish with time remaining, raise you hand and I will come and collect your quiz. You may then work on the lab assignment.

**Good Luck!**

1. (4 points) The truth table below defines a combinational circuit with three inputs (A, B, C) and two outputs (X, Y). Using the **Sum of Products** method, derive a Boolean equation for each output. Use C-style notation:  $\sim$  for NOT,  $|$  for OR, and  $\&$  for AND.

A	B	C	X	Y
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
0	1	1	1	1
1	0	0	0	0
1	0	1	1	0
1	1	0	1	1
1	1	1	0	1

X = \_\_\_\_\_

Y = \_\_\_\_\_

2. (2 points) Which of the following best describes the key difference between a **combinational** circuit and a **sequential** circuit?
  - A. A combinational circuit requires a clock signal; a sequential circuit does not.
  - B. A sequential circuit's output can depend on past inputs (it has memory); a combinational circuit's output depends only on its current inputs.
  - C. A combinational circuit can store data in registers; a sequential circuit cannot.
  - D. A sequential circuit uses only AND and OR gates; a combinational circuit uses all gate types.

3. (2 points) Which expression is equivalent to  $\sim(A \& B)$  according to **DeMorgan's Law**?
- A.  $\sim A \& \sim B$
  - B.  $\sim A \mid \sim B$
  - C.  $A \mid B$
  - D.  $\sim(A \mid B)$
4. (2 points) An edge-triggered D latch (register) captures and stores its input value at what point in the clock cycle?
- A. Continuously, while the clock signal is high (logic 1)
  - B. Continuously, while the clock signal is low (logic 0)
  - C. Briefly, on the rising edge of the clock signal
  - D. Briefly, on the falling edge of the clock signal