

CMPU-224 Lab8 Quiz Solutions

Spring 2025

Name: _____

This is a closed book, closed notes quiz. No electronic devices are allowed. You have until 3:30pm to complete the quiz. There are a total of 4 questions and 10 points.

There should be enough space on the quiz for your answers. If you need more space to work out a problem, blank paper will be available, just ask.

If you finish with time remaining, raise you hand and I will come and collect your quiz. You may then work on the lab assignment.

Good Luck!

1. (4 points) The truth table below defines a combinational circuit with three inputs (A, B, C) and two outputs (X, Y). Using the **Sum of Products** method, derive a Boolean equation for each output. Use C-style notation: \sim for NOT, $|$ for OR, and $\&$ for AND.

A	B	C	X	Y
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
0	1	1	1	1
1	0	0	0	0
1	0	1	1	0
1	1	0	1	1
1	1	1	0	1

X = _____

Y = _____

Solution: Write one AND-term (minterm) per row where the output is 1, then OR them all together. Rows where X=1: (0,1,0), (0,1,1), (1,0,1), (1,1,0). Rows where Y=1: (0,0,1), (0,1,1), (1,1,0), (1,1,1).

$$X = (\sim A \ \& \ B \ \& \ \sim C) \ | \ (\sim A \ \& \ B \ \& \ C) \ | \ (A \ \& \ \sim B \ \& \ C) \ | \ (A \ \& \ B \ \& \ \sim C)$$

$$Y = (\sim A \ \& \ \sim B \ \& \ C) \ | \ (\sim A \ \& \ B \ \& \ C) \ | \ (A \ \& \ B \ \& \ \sim C) \ | \ (A \ \& \ B \ \& \ C)$$

2. (2 points) Which of the following best describes the key difference between a **combinational** circuit and a **sequential** circuit?
- A. A combinational circuit requires a clock signal; a sequential circuit does not.
 - B. A sequential circuit's output can depend on past inputs (it has memory); a combinational circuit's output depends only on its current inputs.**
 - C. A combinational circuit can store data in registers; a sequential circuit cannot.
 - D. A sequential circuit uses only AND and OR gates; a combinational circuit uses all gate types.
3. (2 points) Which expression is equivalent to $\sim(A \ \& \ B)$ according to **DeMorgan's Law**?
- A. $\sim A \ \& \ \sim B$
 - B. $\sim A \ | \ \sim B$**
 - C. $A \ | \ B$
 - D. $\sim(A \ | \ B)$
4. (2 points) An edge-triggered D latch (register) captures and stores its input value at what point in the clock cycle?
- A. Continuously, while the clock signal is high (logic 1)
 - B. Continuously, while the clock signal is low (logic 0)
 - C. Briefly, on the rising edge of the clock signal**
 - D. Briefly, on the falling edge of the clock signal