




# Logic Design

CMPU 224 – Computer Organization  
Jason Waterman
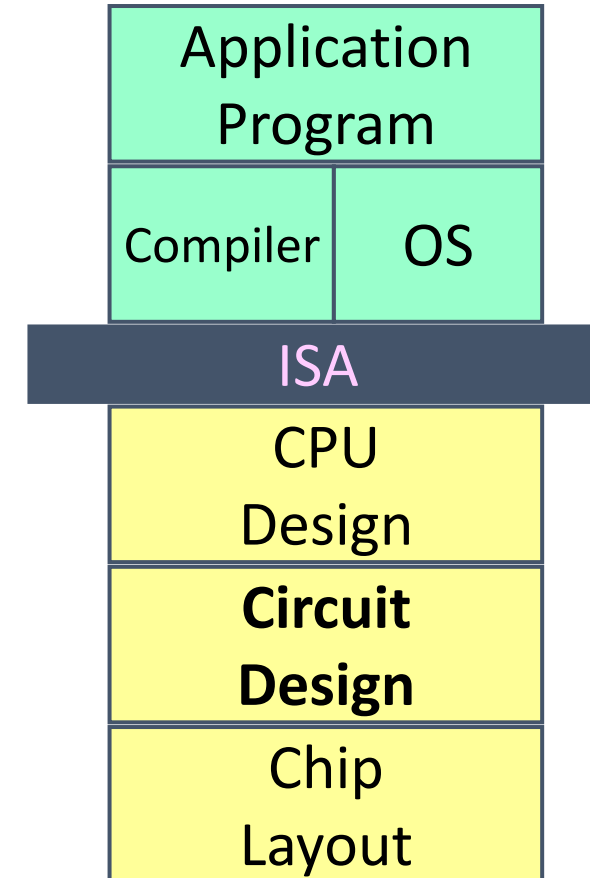
# Overview of Logic Design




- Fundamental Hardware Requirements
  - Communication
    - How to get values from one place to another
  - Computation
  - Storage
- Bits are Our Friends
  - Everything expressed in terms of values 0 and 1
  - Communication
    - Low or high voltage on wire
  - Computation
    - Compute Boolean functions
  - Storage
    - Store bits of information


 
# Digital Signals




- Use voltage thresholds to extract discrete values from continuous signal
- Simplest version: 1-bit signal
  - Either high range (1) or low range (0)
  - With guard range between them
- Not strongly affected by noise or low-quality circuit elements
  - Can make circuits simple, small, and fast


 
# Computing with Logic Gates




- Outputs are Boolean functions of inputs
- Respond continuously to changes in inputs
  - With some small delay


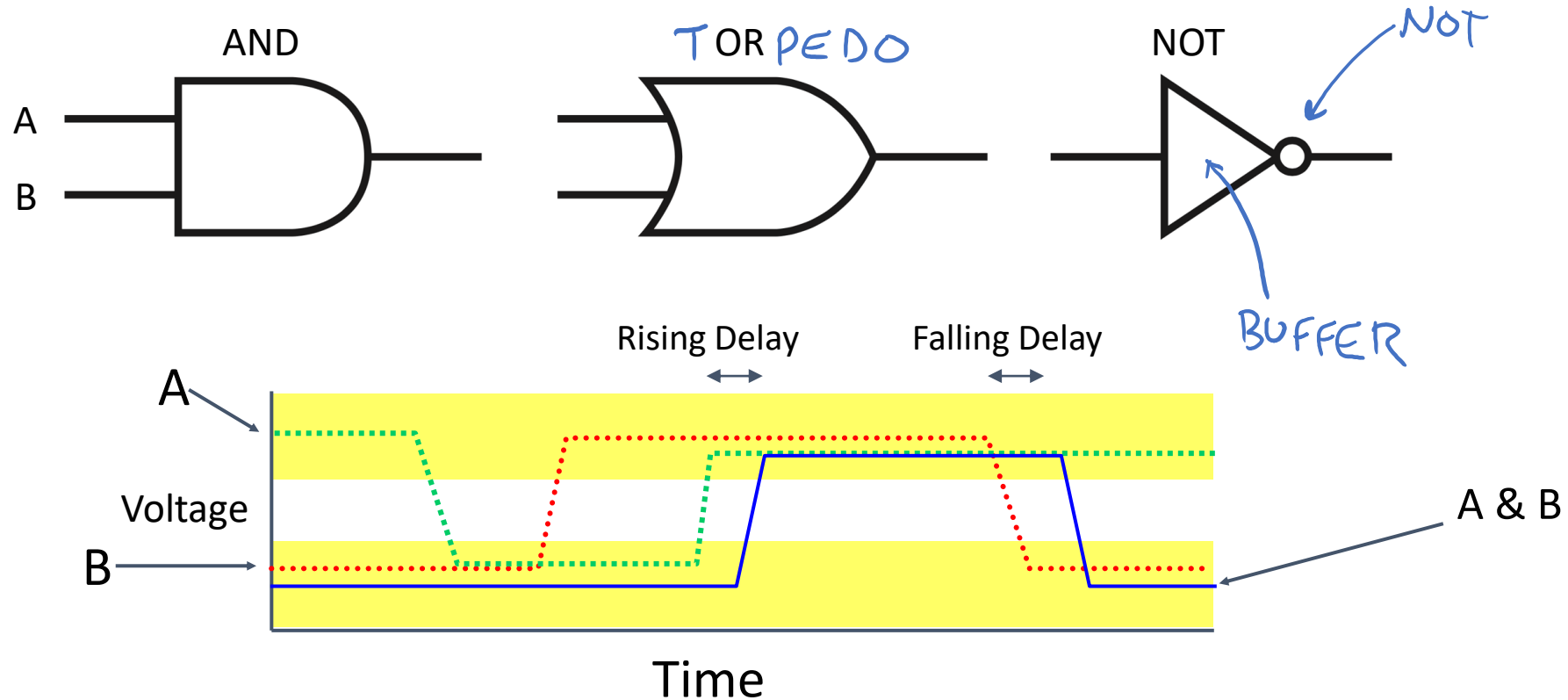
# Computing with Logic Gates





- Outputs are Boolean functions of inputs
- Respond continuously to changes in inputs
  - With some small delay


 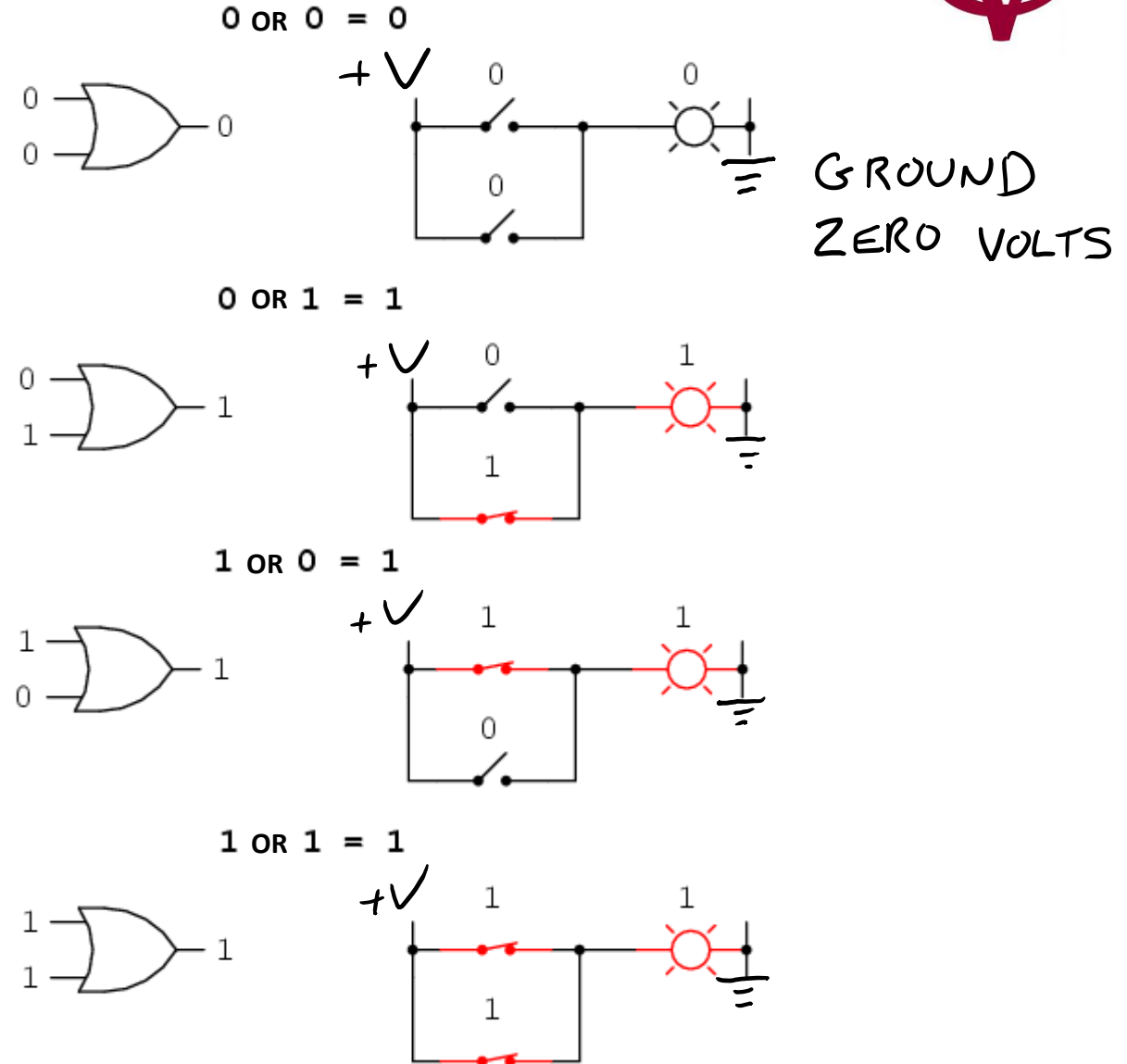
# What's a logic gate?




- They are referred to as logic gates because of their ability to “open” and “close” pathways for signals
  - Made up of transistors which act as tiny switches
- OR gate shown on the right, AND gate shown below


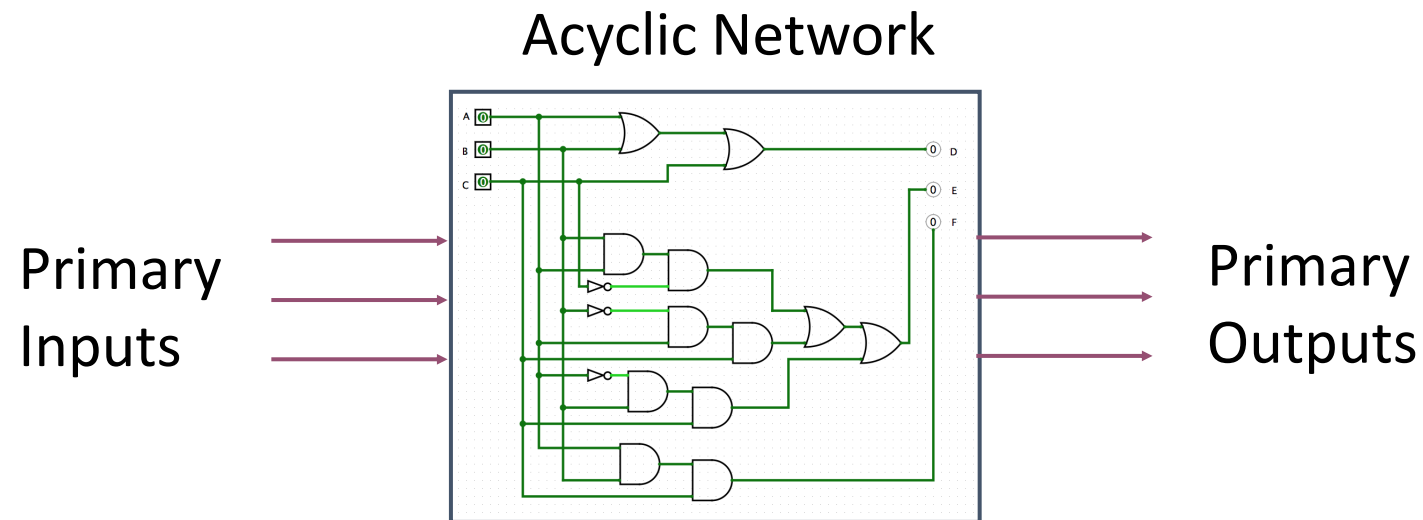
# Combinational Circuits



- Acyclic Network of Logic Gates
  - Continuously responds to changes on primary inputs
  - Primary outputs become (after some delay) Boolean functions of primary inputs
  - Output is solely dependent on the current input (no memory)





# Truth Tables

- Combinational logic blocks can be completely specified by defining the values of the outputs for each possible set of input values
- For a logic block of  $n$  inputs there are  $2^n$  entries in the truth table
- Can completely describe any combinational circuit, but it quickly grows in size

Inputs			Outputs		
A	B	C	D	E	F
0	0	0	0	0	0
0	0	1	1	0	0
0	1	0	1	0	0
0	1	1	1	1	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	0
1	1	1	1	0	1

# Boolean Algebra



- Often easier to express logic function with logic equations instead of truth table
- Use Boolean algebra
  - All variables have the values 0 or 1
  - Three operators:
    - OR, written as  $|$  (e.g.,  $A | B$ ) and its output is 1 if either of the variables is 1
    - AND, written as  $\&$  (e.g.,  $A \& B$ ) and its output is 1 only if both variables are 1
    - NOT, a unary operator written as  $!$  (e.g.,  $!A$ ) and its output is 1 only if the input is 0

# Logic Equations



- **Any** combinational circuit can be written as a series of Boolean equations
- $\text{OutputVar} = \text{Boolean Equation of InputVars}$
- In the previous truth table:
  - D is one when at least one of the inputs is 1
  - E is one when exactly two inputs are 1
  - F is one when all three inputs are 1
- This truth table can be written as:
  - $D = A \mid B \mid C$
  - $E = (A \ \& \ B \ \& \ !C) \mid (A \ \& \ !B \ \& \ C) \mid (!A \ \& \ B \ \& \ C)$
  - $F = A \ \& \ B \ \& \ C$

Inputs			Outputs		
A	B	C	D	E	F
0	0	0	0	0	0
0	0	1	1	0	0
0	1	0	1	0	0
0	1	1	1	1	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	0
1	1	1	1	0	1



# Sum of Products

- **Any** logic function can be implemented with only AND, OR, and NOT functions
- Can be written as a two-level representation as a logical **sum of products**

- Logical sum: OR
  - $0 + 0 = 0$
  - $0 + 1 = 1$
  - $1 + 0 = 1$
  - $1 + 1 = 1$
- Logical product: AND
  - $0 * 0 = 0$
  - $0 * 1 = 0$
  - $1 * 0 = 0$
  - $1 * 1 = 1$

Inputs			Outputs		
A	B	C	D	E	F
0	0	0	0	0	0
0	0	1	1	0	0
0	1	0	1	0	0
0	1	1	1	1	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	0
1	1	1	1	0	1

## Example:


- $E = (!A \& B \& C) \mid (A \& !B \& C) \mid (A \& B \& !C)$
- $F = A \& B \& C$
- $D = (!A \& !B \& C) \mid (!A \& B \& !C) \mid (!A \& B \& C) \mid \cancel{(A \& !B \& !C)} \mid \cancel{(A \& !B \& C)} \mid \cancel{(A \& B \& !C)} \mid \cancel{(A \& B \& C)}$

$(A \& !B)$

$(A \& B)$

- Sum of products does not always produce the simplest logic circuit that could implement the function!

# Truth Table Implementation



 


# Equality



A	B	eq
0	0	1
0	1	0
1	0	0
1	1	1

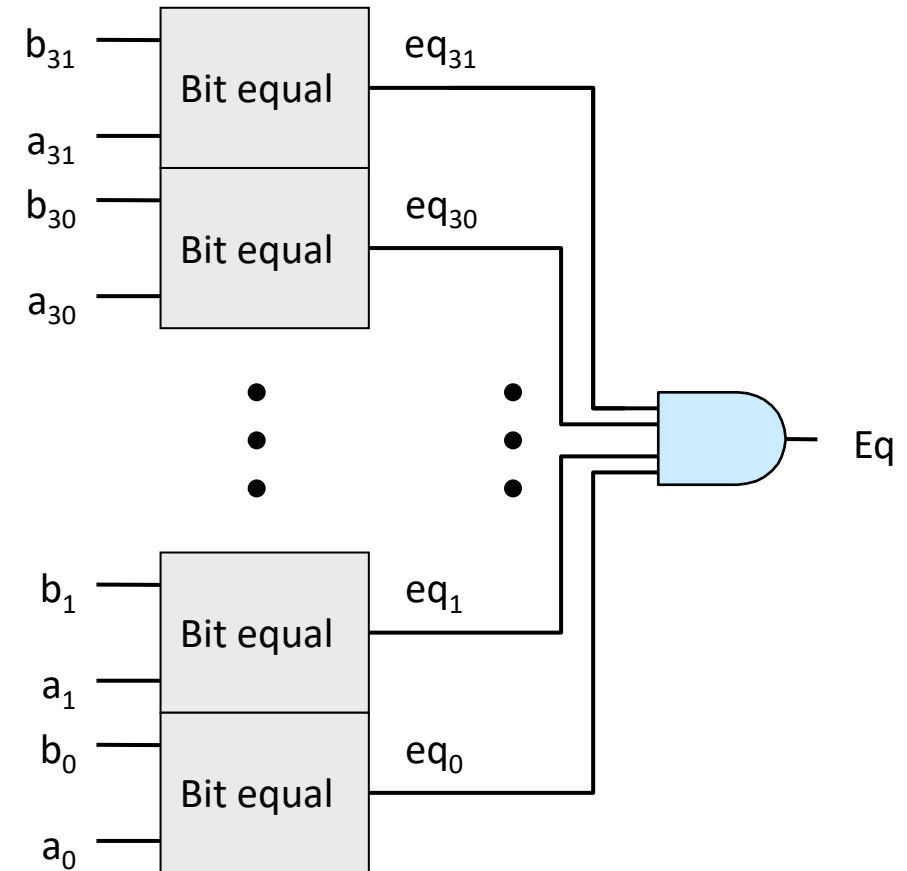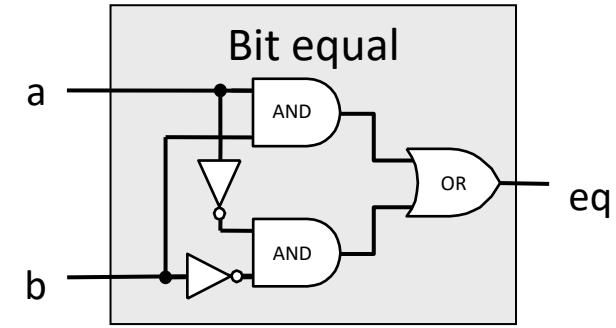 - Generate 1 if a and b are equal
- Word equality
  - A and B both represent 32-bit words
    - represented by bold line
  - Eq is a 1-bit 'boolean'
    - represented by a dashed line








# Bit-Level Multiplexor

- Control signal  $s$
- Data signals  $A$  and  $B$
- Output **A** when  $s=1$ , **B** when  $s=0$

## Word-Level Representation

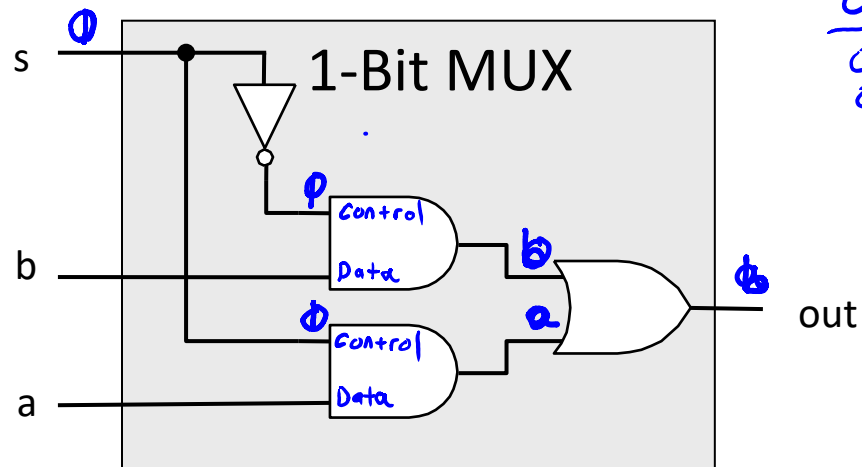 


C	D	Out
0	0	0
0	1	1
1	0	0
1	1	1

 


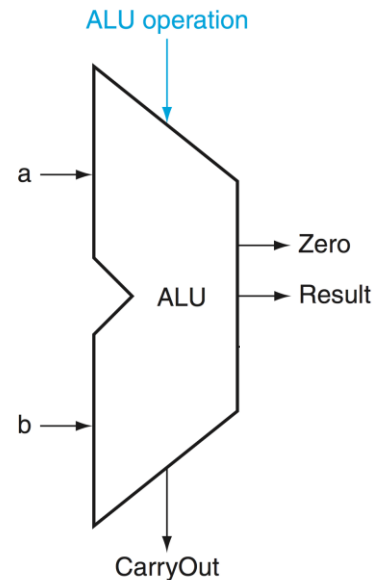
# Arithmetic Logic Unit


- Arithmetic Logic Unit (ALU) is the heart of the processor
  - Performs arithmetic operations (addition, subtraction, etc.)
  - Performs logical operations (and, or, not, shifts, etc.)
- We can build a 32-bit ALU with the combinational blocks previously mentioned
- Operations:
  - Bitwise AND
  - Bitwise OR
  - Addition
  - Subtraction
- Flags:
  - Zero
  - Carryout




 
# First Steps: A 1-Bit ALU

- General idea: Build a 1-bit ALU and duplicate it 32 times
- Start with logical operations which map directly to logic gates
- Simple 1-bit logical unit for AND and OR
- Operation is an input to a multiplexor which decides the result






# 1-Bit Half Adder

- Like to add two 1-bit numbers A and B
  - Will generate two outputs:
    - Sum (A+B)
    - CarryOut



A	B	CarryOut	(A+B) Sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

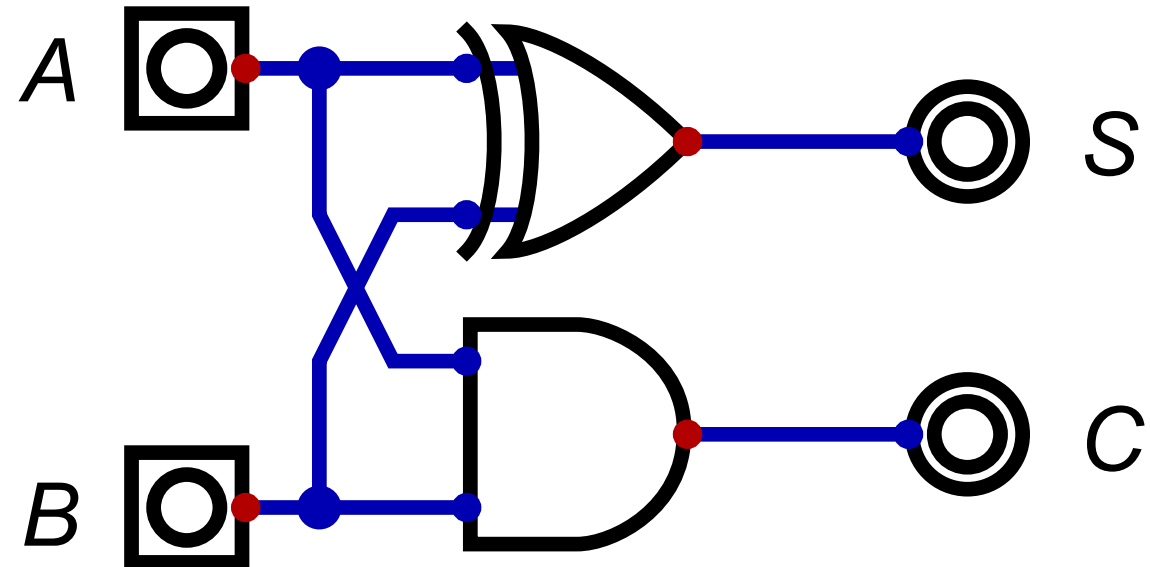
  
# 1-Bit Full Adder




- Also called a 3,2 adder because it has three inputs and two outputs
- Can be built from 2 half adders
  - First half adder computes sum of  $A+B$
  - Second half adder sum of  $C_{in}$  and  $(A+B)$
- If either addition generates a CarryOut, propagate it forward as  $C_{out}$




**4-Bit Ripple Adder**

Inputs			Outputs		Comments
a	b	CarryIn	CarryOut	Sum	
0	0	0	0	0	$0 + 0 + 0 = 00_{two}$
0	0	1	0	1	$0 + 0 + 1 = 01_{two}$
0	1	0	0	1	$0 + 1 + 0 = 01_{two}$
0	1	1	1	0	$0 + 1 + 1 = 10_{two}$
1	0	0	0	1	$1 + 0 + 0 = 01_{two}$
1	0	1	1	0	$1 + 0 + 1 = 10_{two}$
1	1	0	1	0	$1 + 1 + 0 = 10_{two}$
1	1	1	1	1	$1 + 1 + 1 = 11_{two}$

# A 1-Bit ALU

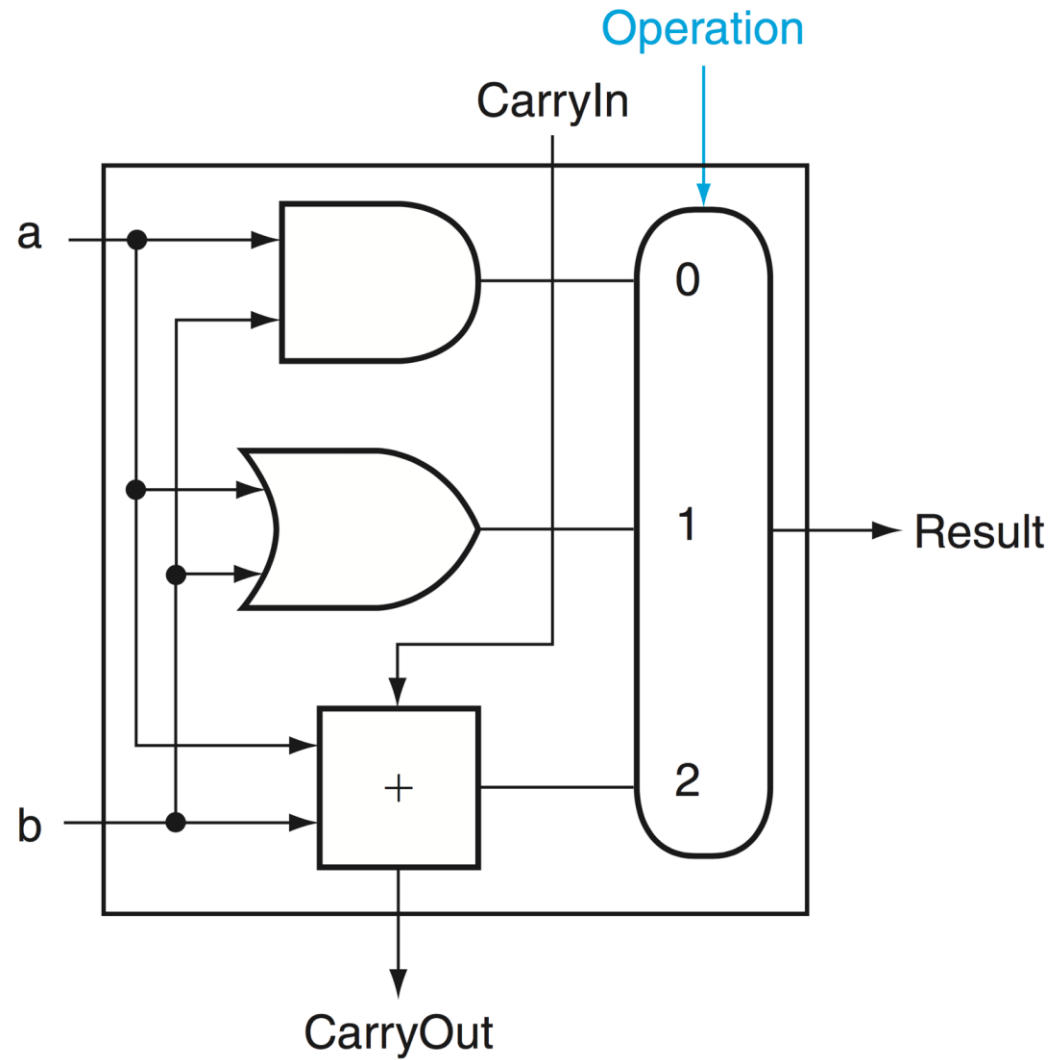


# 32-Bit ALU

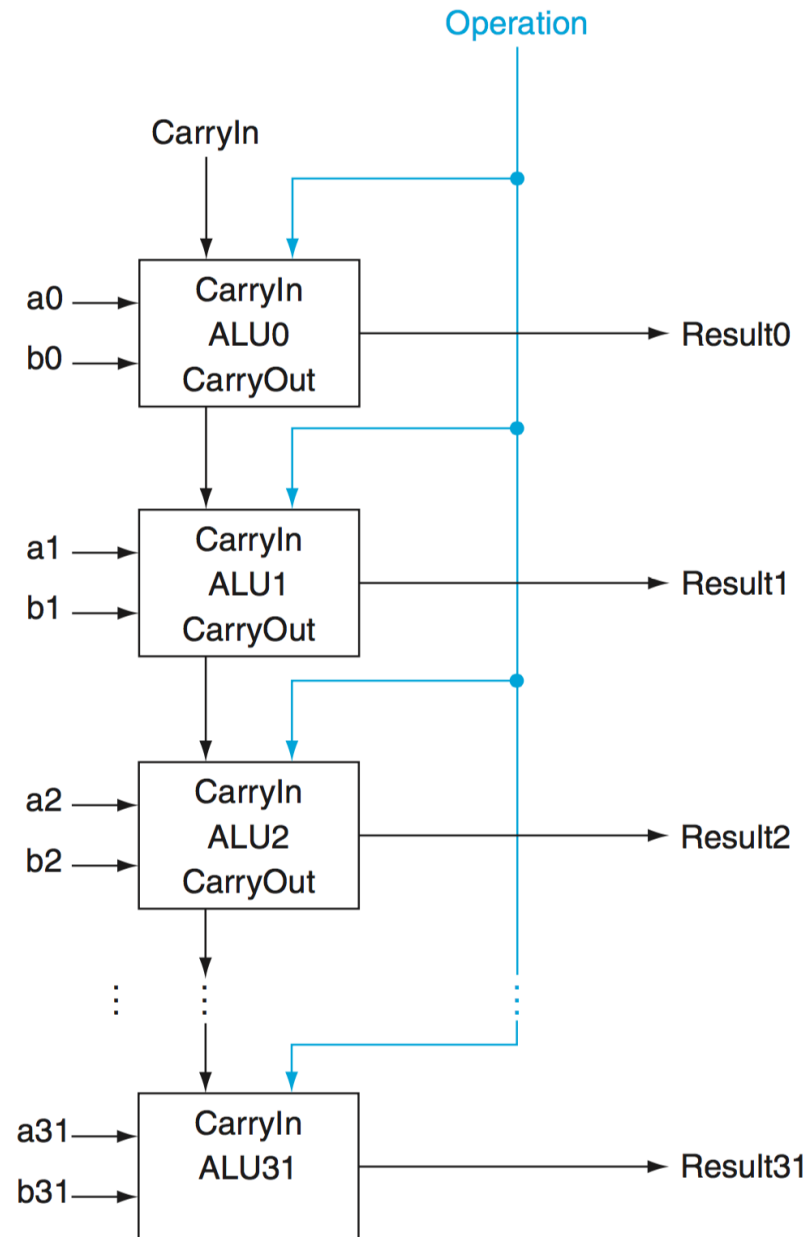
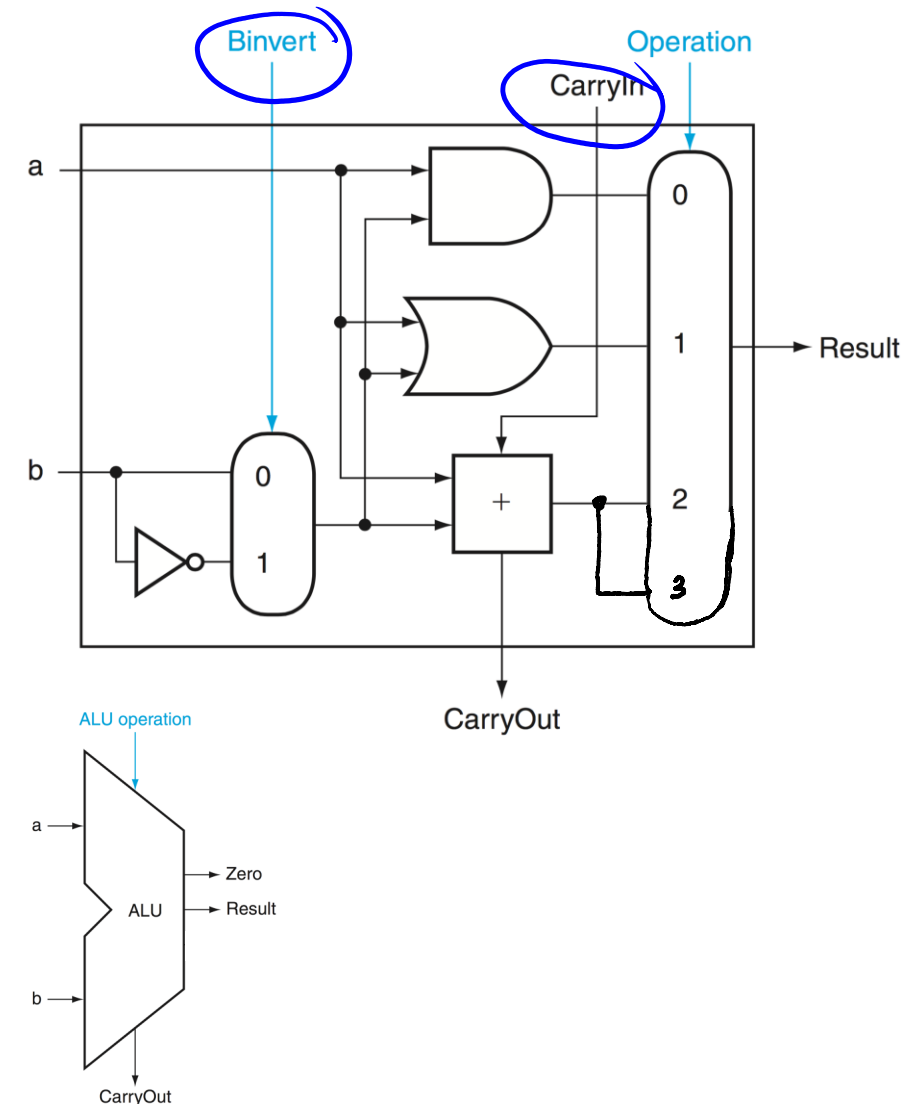
# Adding Subtraction and Flags to the ALU



- To subtract  $a - b$ , we take the two's complement of  $b$  and add
  - Two's complement of  $b$  is  $\sim b + 1$
  - Set `Binvert` and `CarryIn` to 1 (use lower bit of `Operation` signal)
- Flags
  - `CarryOut` – Use the `CarryOut` bit of the 32<sup>nd</sup> 1-bit adder
  - `Zero` – Or the 32 bits of the result together
- ALU Operation (2-bits)
  - 00 – And
  - 01 – OR
  - 10 – ADD
  - 11 – SUB
- Where does the `Operation` bits come from?
  - Directly from the encoding of the machine language instruction



# Summary



- The ALU (Arithmetic Logic Unit) of a CPU is composed of Digital Logic Circuits
  - Logic gates connected in an acyclic graph
  - Treat as a deterministic black box
  - With a given input, you will get a given output (after a short time delay)
- Any truth table or Boolean equation can be implemented as a logic circuit
  - Sum of Products is one foolproof way to convert to a circuit
  - Will be correct, but not necessarily the smallest possible circuit
- More complex circuits are built out of smaller building blocks
- CPU development is done at a higher level than this (VHDL, Verilog)
  - Software tools convert high-level logic to circuit diagrams
- Next time: How registers are implemented