



Sequential Logic


CMPU 224 – Computer Organization
Jason Waterman

Sequential Logic Intro



- Last time: **Combinational Circuits**

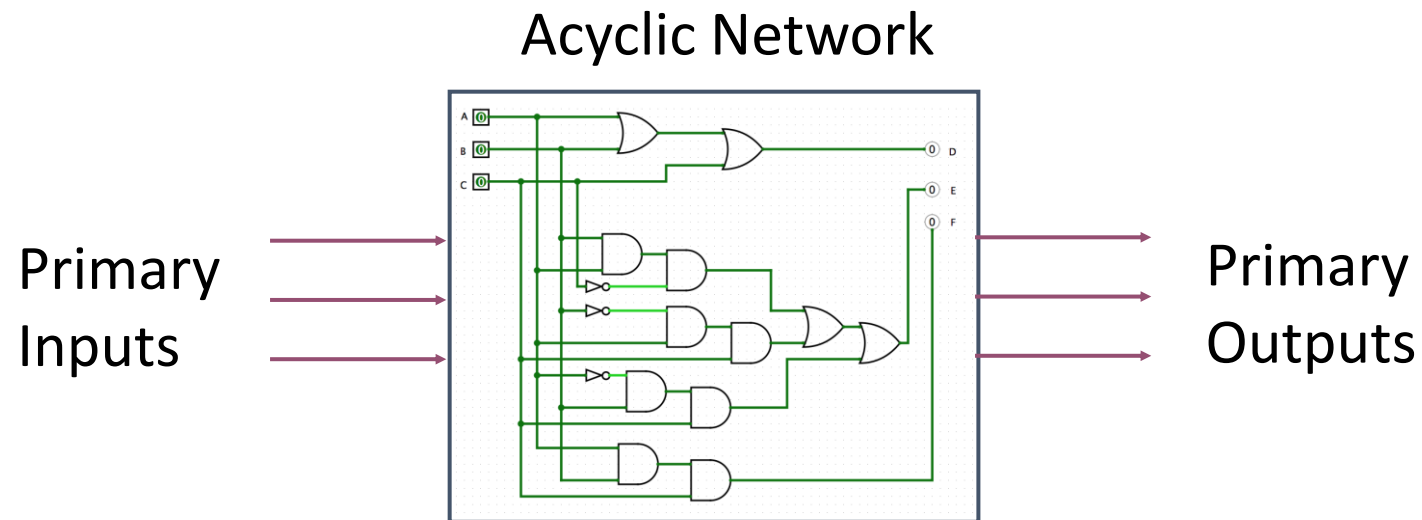
- Acyclic Network of Logic Gates
- Continuously responds to changes on primary inputs
- Primary outputs become (after some delay) Boolean functions of primary inputs





Sequential Logic




 
- Sequential logic circuits are those whose outputs are also dependent upon past inputs
- In other words, the output of a sequential circuit may depend upon its previous outputs
- In effect, it has some form of "memory"





Storing 1 Bit

  

Storing 1 Bit

  


Physical Analogy

  

Storing and Accessing 1 Bit




Bistable Element

 


$q = 0 \text{ or } 1$




Storing

 

Resetting

 


Setting

 

Reset-Set Latch


R-S Latch

 

1-Bit Latch




D Latch

 


R	S	State
1	0	Reset to 0
0	1	Set to 1
0	0	Storing

d	R	S
0	1	0
1	0	1


Storing

 


Latching

 

Clocking

 

R	S	State
1	0	Reset to 0
0	1	Set to 1
0	0	Storing

 





Transparent 1-Bit Latch

- When in latching mode, combinational propagation from D to Q+ and Q-
- Value latched depends on value of D as C falls


Latching

 

Changing D

 


Edge-Triggered Latch

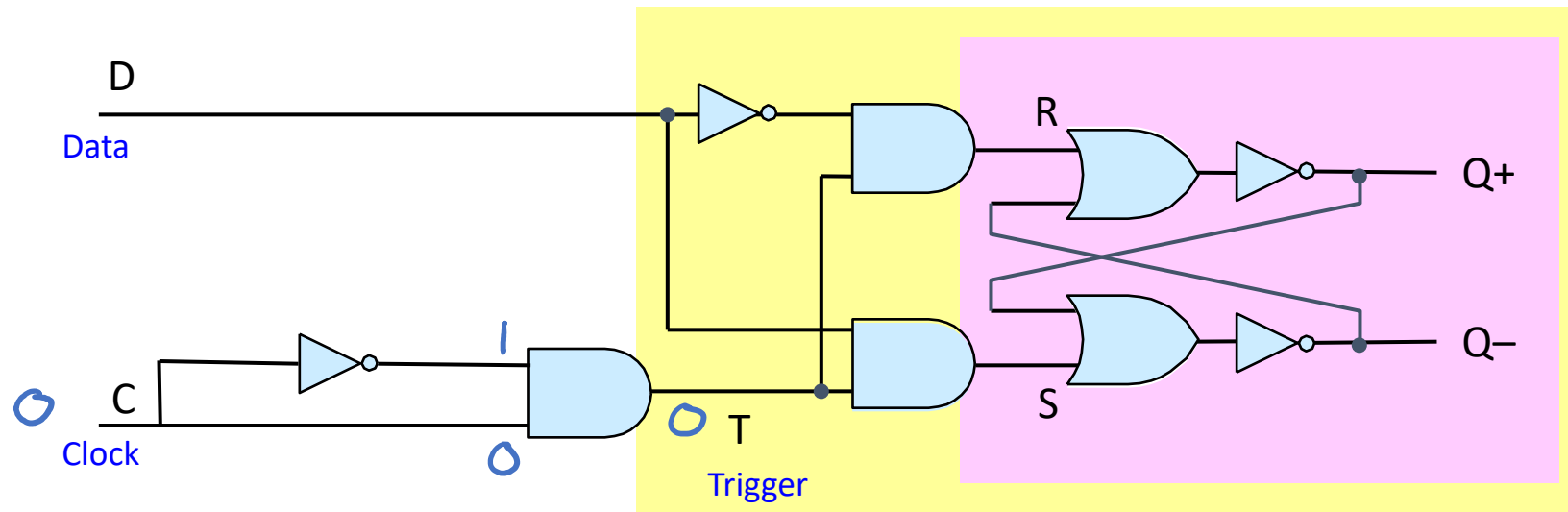

CLOCK
LOW


STORAGE
MODE

INPUT D
IS IGNORED

 

- Only in latching mode for brief period
 - Rising clock edge
- Value latched depends on the data as the clock rises
- Output remains stable at all other times

Edge-Triggered Latch

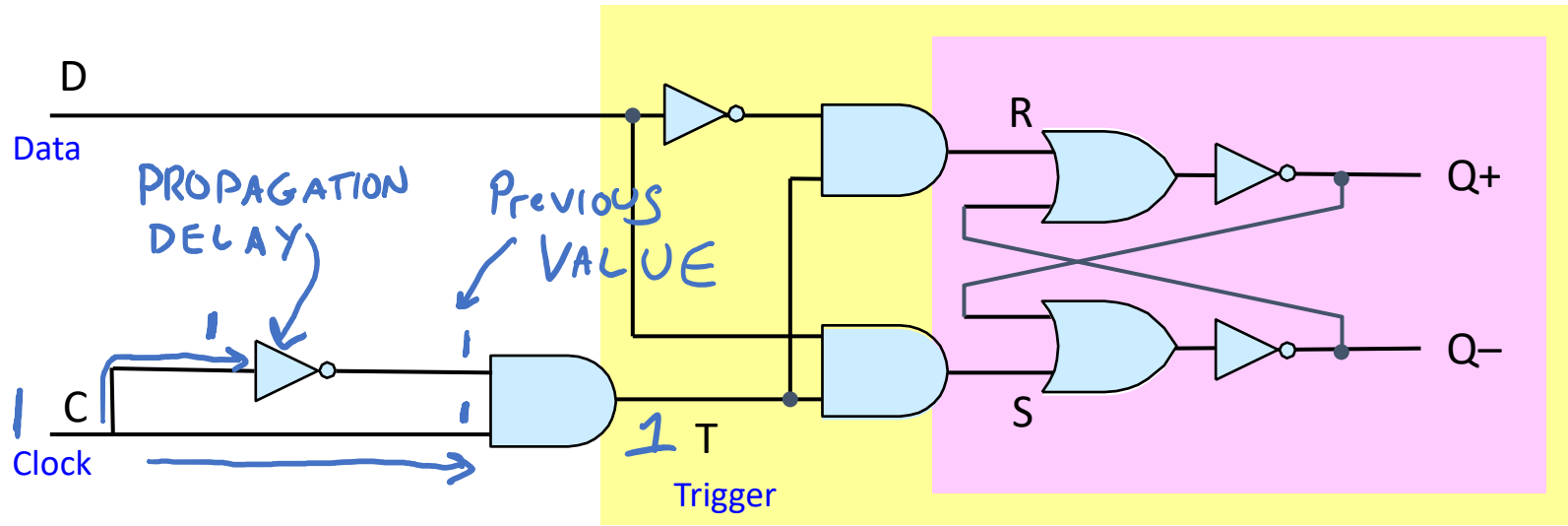


RISING
CLOCK
EDGE




0 → 1

TRIGGER
IS BRIEFLY
1: LATCHING MODE

 


- Only in latching mode for brief period
 - Rising clock edge
- Value latched depends on the data as the clock rises
- Output remains stable at all other times

Edge-Triggered Latch

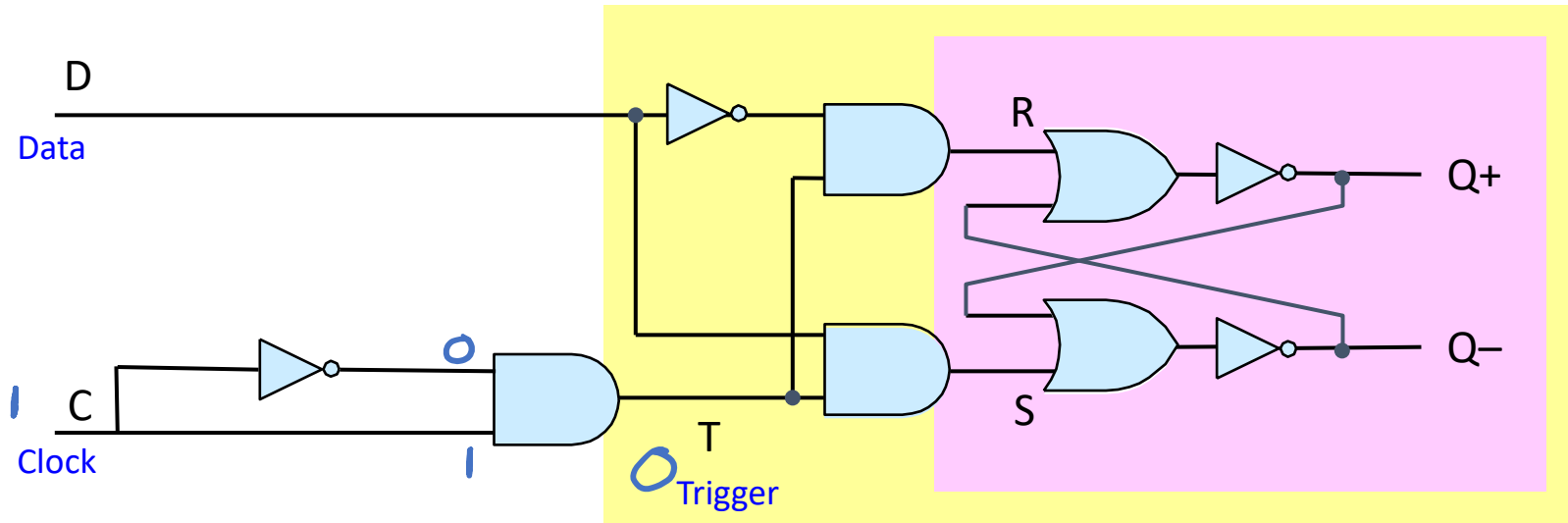

CLOCK HIGH

INPUT D IS IGNORED

 



- Only in latching mode for brief period
 - Rising clock edge
- Value latched depends on the data as the clock rises
- Output remains stable at all other times

FOR THE REST OF THE CLOCK CYCLE !!!

Registers



 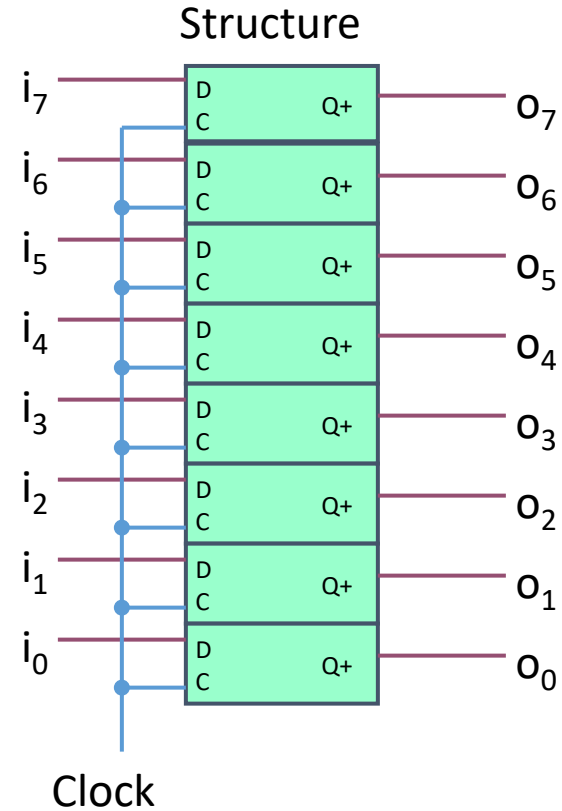
- Stores a word of data
- Collection of edge-triggered latches
- Loads input on rising edge of clock



Register Operation



 
- Stores data bits
- Most of the time it acts as barrier between input and output
- At the rising edge of the clock, it loads its input



Random-Access Memory




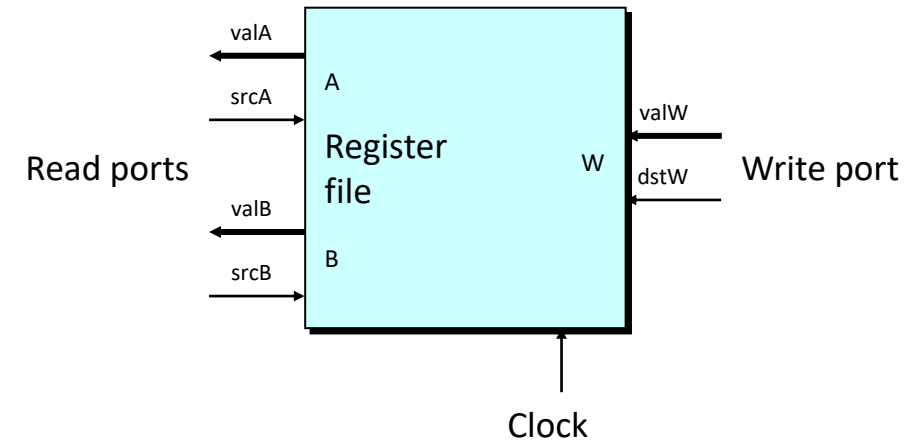
- Stores multiple words of memory
 - Address input specifies which word to read or write
- Register file
 - Holds values of program registers
 - `a0`, `ra`, etc.
 - Register identifier serves as index into the register file
- Multiple Ports
 - Can read and/or write multiple words in one cycle
 - Each has separate address and data input/output



Register File Timing



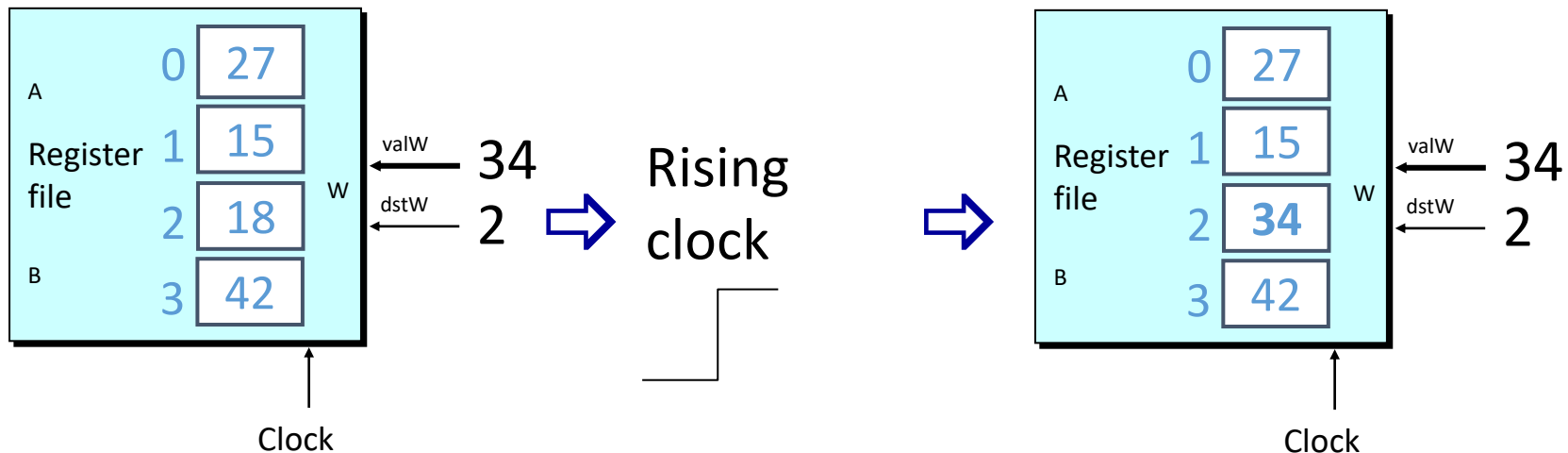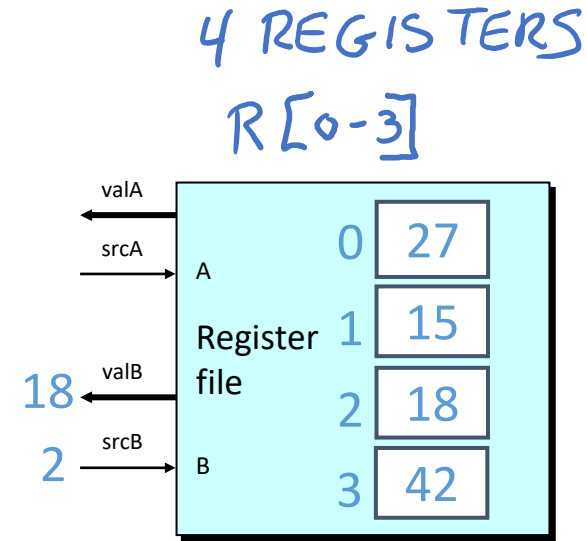- Reading
 - Like combinational logic
 - Output data generated based on input address
 - After some delay
- Writing
 - Like a register
 - Update only as clock rises



Summary



- Computation
 - Performed by combinational logic
 - Computes Boolean functions
 - Continuously reacts to input changes
- Storage
 - Registers
 - Hold single words
 - Loaded as clock rises
 - Random-access memories
 - Hold multiple words
 - Possible multiple read or write ports
 - Read word when address input changes
 - Write word as clock rises