



# The RV32I Single-Cycle Processor

CMPU 224 – Computer Organization  
Jason Waterman

# RISC-V Instruction Formats



- Six types of instruction formats
  - Opcode bits specify which type
- Needed because all instructions are 32 bits long
- Opcode, rs1, rs2, rd, and funct3 are always located in the same bit positions
- Immediate bits are scrambled among the different instruction types
  - Needed to keep rs1, rs2, and rd at a fixed location across instructions
  - Bit-31 is always the sign bit of the immediate value



B and J immediates are scrambled across fields (bit 0 always implicit zero — targets are 2-byte aligned).  
rs1, rs2, rd always live in bits [19:15], [24:20], [11:7] — same positions in every format that uses them.

RISC-V RV32I Instruction Formats

# RISC-V Instructions: R-type (Register-Register)



- Both operands come from registers (rs1 and rs2)
- Result goes to a register (rd)
- The funct7 and funct3 fields together select the operations
- Used by arithmetic and logic instructions
  - Examples: add, sub, and, or, slt, sll, srl, sra



B and J immediates are scrambled across fields (bit 0 always implicit zero — targets are 2-byte aligned).  
rs1, rs2, rd always live in bits [19:15], [24:20], [11:7] — same positions in every format that uses them.

RISC-V RV32I Instruction Formats

# RISC-V Instructions: I-type (Immediate)



- Used in instructions with one register operand and an immediate
- The immediate is a 12-bit two's complement number sign-extended to 32 bits before use
- Examples:
  - loads (lw, lb) – the memory address of the load is calculated by  $rs1 + imm$
  - Arithmetic with a constant (addi, andi, ori)
  - Jump and link register (jalr) – jump address is  $rs1 + imm$



B and J immediates are scrambled across fields (bit 0 always implicit zero — targets are 2-byte aligned).  
rs1, rs2, rd always live in bits [19:15], [24:20], [11:7] — same positions in every format that uses them.

RISC-V RV32I Instruction Formats

# RISC-V Instructions: S-type (Store)



- Stores a register value to memory
- The immediate is split across two fields
  - Keeps rs1 and rs2 in the same position
- Examples:
  - sw, sb



B and J immediates are scrambled across fields (bit 0 always implicit zero — targets are 2-byte aligned).  
 rs1, rs2, rd always live in bits [19:15], [24:20], [11:7] — same positions in every format that uses them.

RISC-V RV32I Instruction Formats

# RISC-V Instructions: B-type (Branch)



- Conditional branches
- 12-bit signed offset represents a 13-bit offset from the PC
  - Known as PC-relative addressing
  - Has an implied lsb of 0
  - All RISC-V instructions must start on an address that is multiple of 2
  - Range: +/- 4KiB
- bit-31 is the sign bit
- Other immediate bits are scrambled to overlap with S-type instructions
- Examples:
  - beq, bne, blt, bge




B and J immediates are scrambled across fields (bit 0 always implicit zero — targets are 2-byte aligned).  
rs1, rs2, rd always live in bits [19:15], [24:20], [11:7] — same positions in every format that uses them.

RISC-V RV32I Instruction Formats
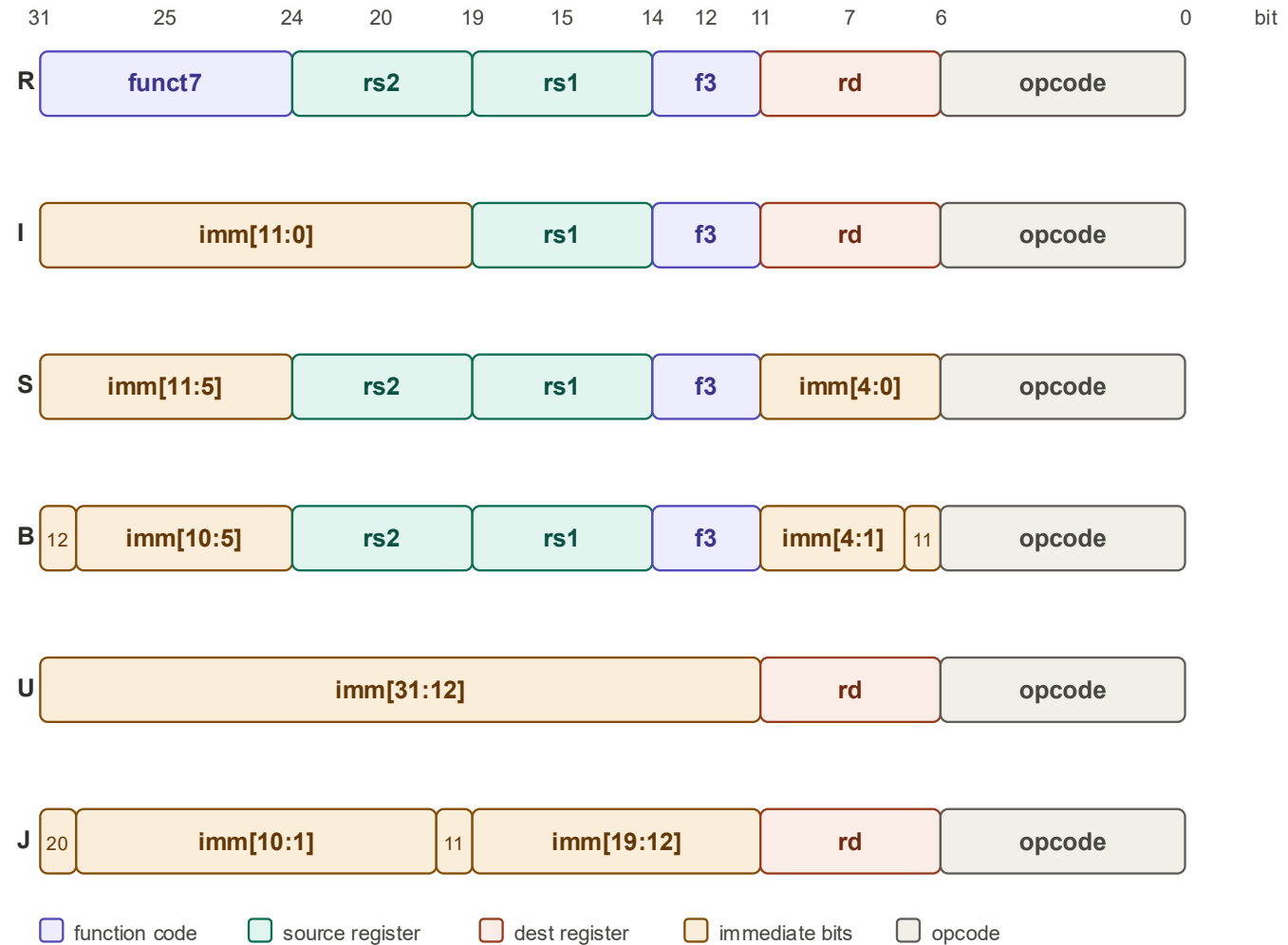
# RISC-V Instructions: U-type (Upper Immediate)



- Loads a 20-bit constant into the upper 20 bits of a register
- Typically paired with an I-type instruction (addi) to build a 32-bit constant or 32-bit address
- Instructions:
  - lui – load upper immediate
  - auipc – add upper immediate to PC



B and J immediates are scrambled across fields (bit 0 always implicit zero — targets are 2-byte aligned).  
 rs1, rs2, rd always live in bits [19:15], [24:20], [11:7] — same positions in every format that uses them.

RISC-V RV32I Instruction Formats

# RISC-V Instructions: J-type (Jump)



- Used only be jal (jump and link)
- Encodes a 21-bit signed offset
  - Also has implicit zero in bit zero
- Range: +/- 1 MiB
- Scrambled imm value to overlap with B-type instructions
- rd receives the return address (PC + 4)





B and J immediates are scrambled across fields (bit 0 always implicit zero — targets are 2-byte aligned).  
 rs1, rs2, rd always live in bits [19:15], [24:20], [11:7] — same positions in every format that uses them.

RISC-V RV32I Instruction Formats


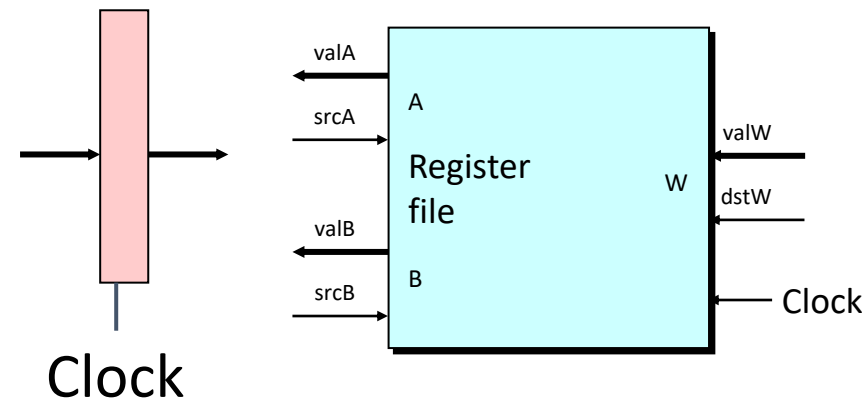 
# Building Blocks

- Combinational Logic
  - Compute Boolean functions of inputs
  - Continuously respond to input changes
  - Operate on data and implement control
- Storage Elements
  - Store bits
  - Registers
  - Addressable memories
  - Loaded only as clock rises





# Processor State

- There are four categories of state that are updated each clock cycle
  1. Program Counter (PC)
    - 32-bit register holding the address of the current instruction
    - Updated every cycle to the next instruction address
  2. Register File
    - 32 registers x 32 bits
    - Two read ports (rs1, rs2) and one write port (rd)
    - Register x0 is hardwired to zero
    - Read is combinational; write happens on the rising edge of the clock
  3. Instruction Memory
    - Addressed by PC
    - Outputs the 32-bit instruction
    - Considered read-only memory
  4. Data Memory
    - Used by load and store instructions
    - One address input, one write-data input, one read-data output

# Single-Cycle Datapath Overview




- Even though the single-cycle processor executes an instruction in one clock cycle, we conceptually divide execution into five stages
  1. Fetch (IF)
    - Read instruction from instruction memory at address PC
    - Compute PC+4 (next instruction)
  2. Decode (ID)
    - Read source registers rs1 and rs2
    - Generate immediate
    - Decode control signals
  3. Execute (EX)
    - Alu performs operation (arithmetic, address calculation, or comparison)
  4. Memory (MEM)
    - Read from or write to memory (loads and stores only)
  5. Writeback (WB)
    - Write result back to the destination register rd
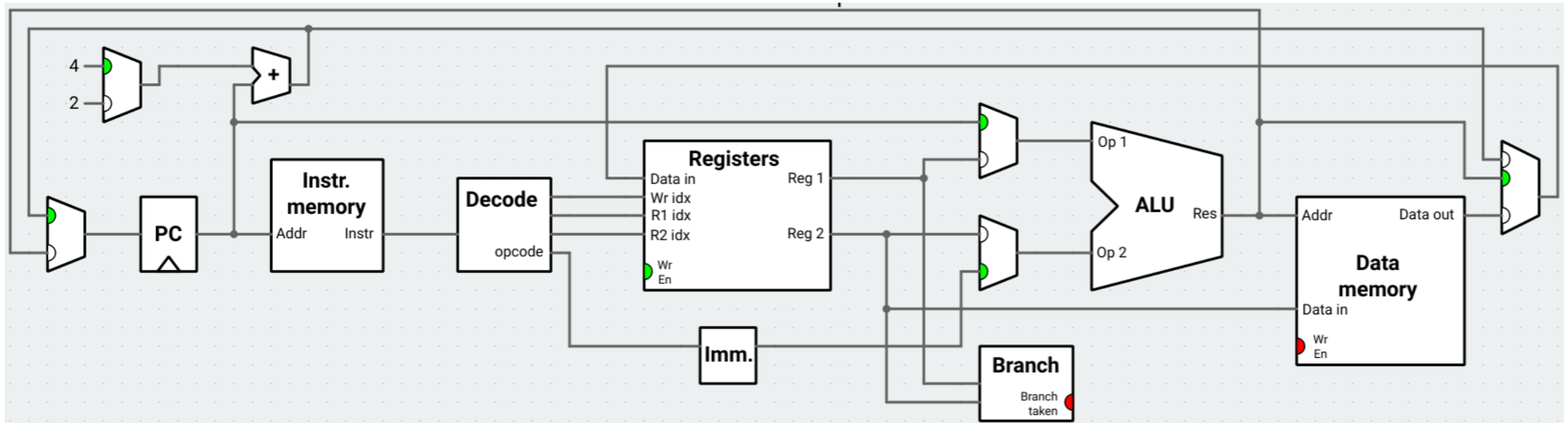
# Datapath Diagram




- Data flows from left to right through each of the stages
- Control signals (not shown) from the Decode stage to every other stage, telling the muxes and functional units what to do


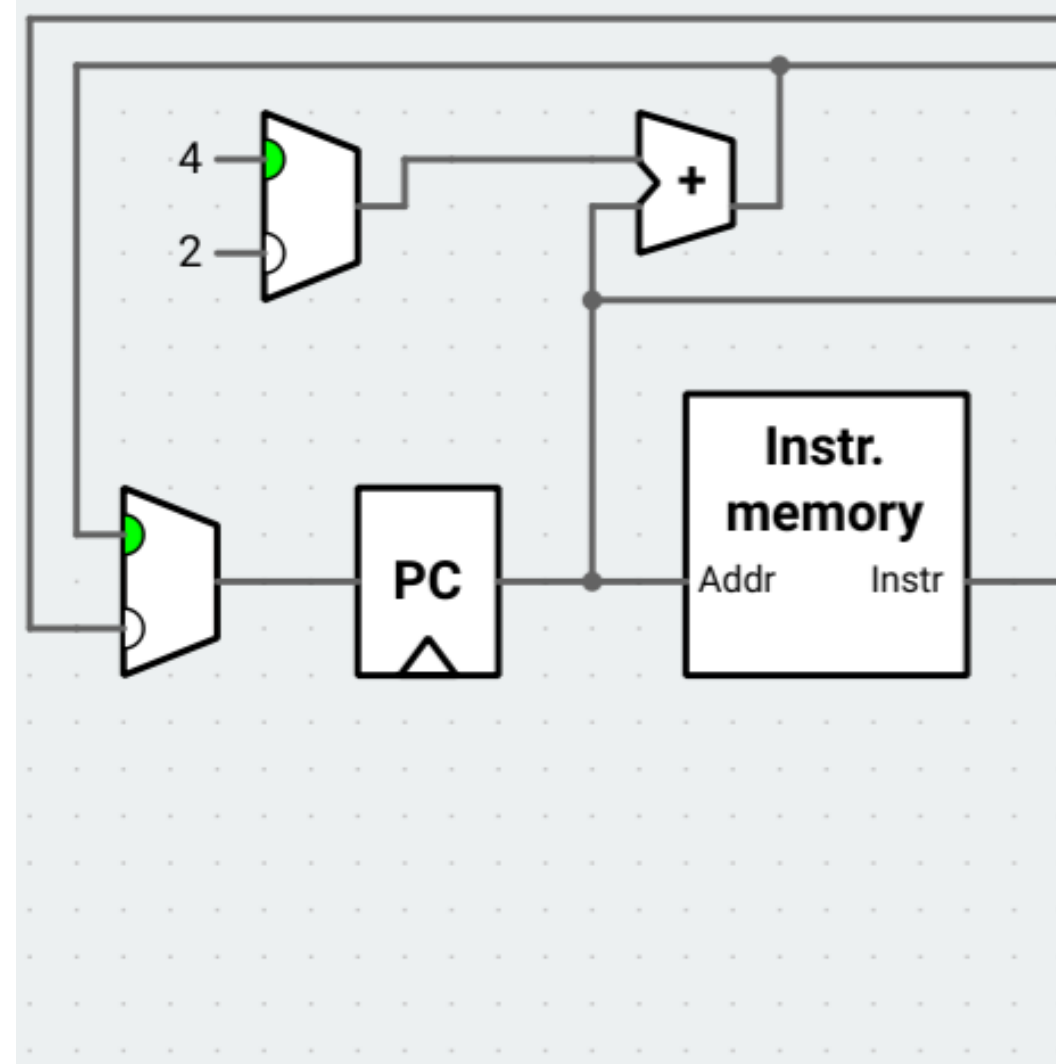
# Fetch Stage (IF)


- Read the current instruction and compute the address of the next one
- The PC supplies the address to Instruction Memory
- Instruction Memory outputs the 32-bit instruction word
- Mux selects the next PC value
  - PC+4 for sequential execution
  - Branch target (PC+imm) if branch is taken (from ALU)
  - Jump target for jal / jalr (from ALU)




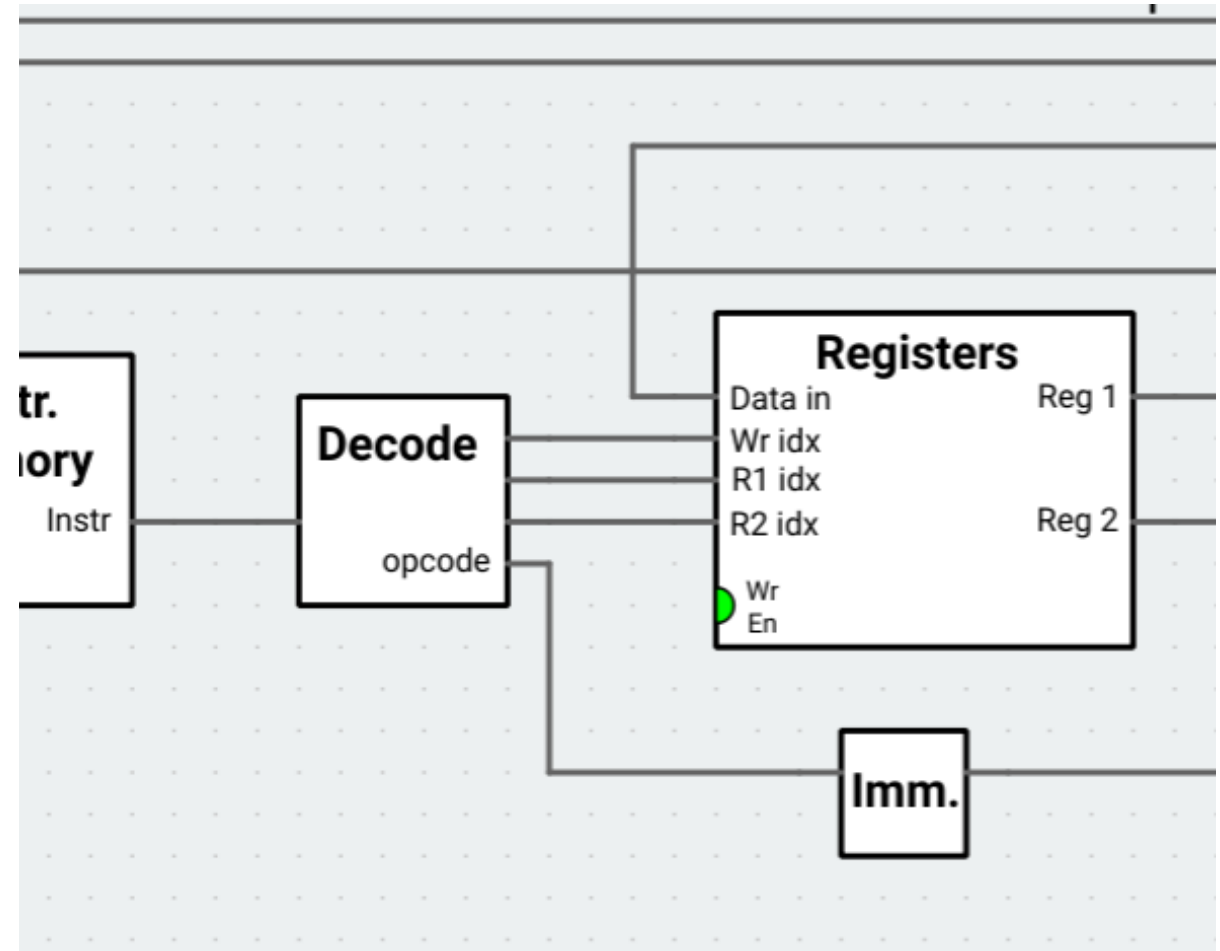
# Decode Stage (ID)


- Extract register specifiers, generate the immediate value, read the register file, and produce control signals (not shown)
- The **Immediate Generator** extracts and sign-extends the immediate based on instruction format (I, S, B, U, J)
- The **Register File** reads values at addresses rs1 and rs2, producing ReadData1 and ReadData2




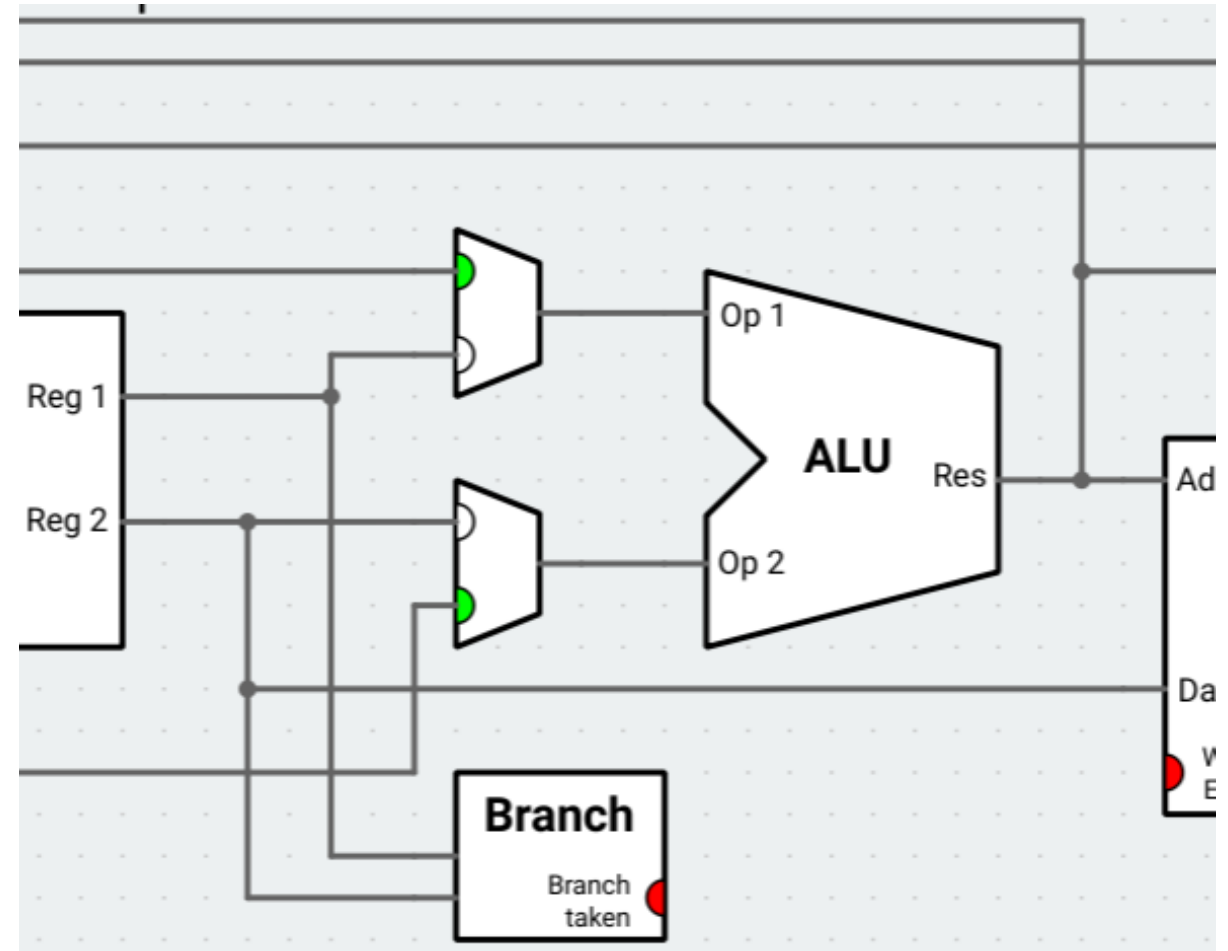
# Execute Stage (EX)


- Perform the computation
  - Arithmetic, logic, address, or branch comparison
- The **ALU** receives two inputs:
  - **Op1**: ReadData1 (value of rs1) or PC
  - **Op2**: ReadData2 (value or rs2) or the sign-extended **immediate**
- The **Branch** logic is a separate adder for comparison
  - Generates a Boolean whether the branch should be taken for comparison instructions




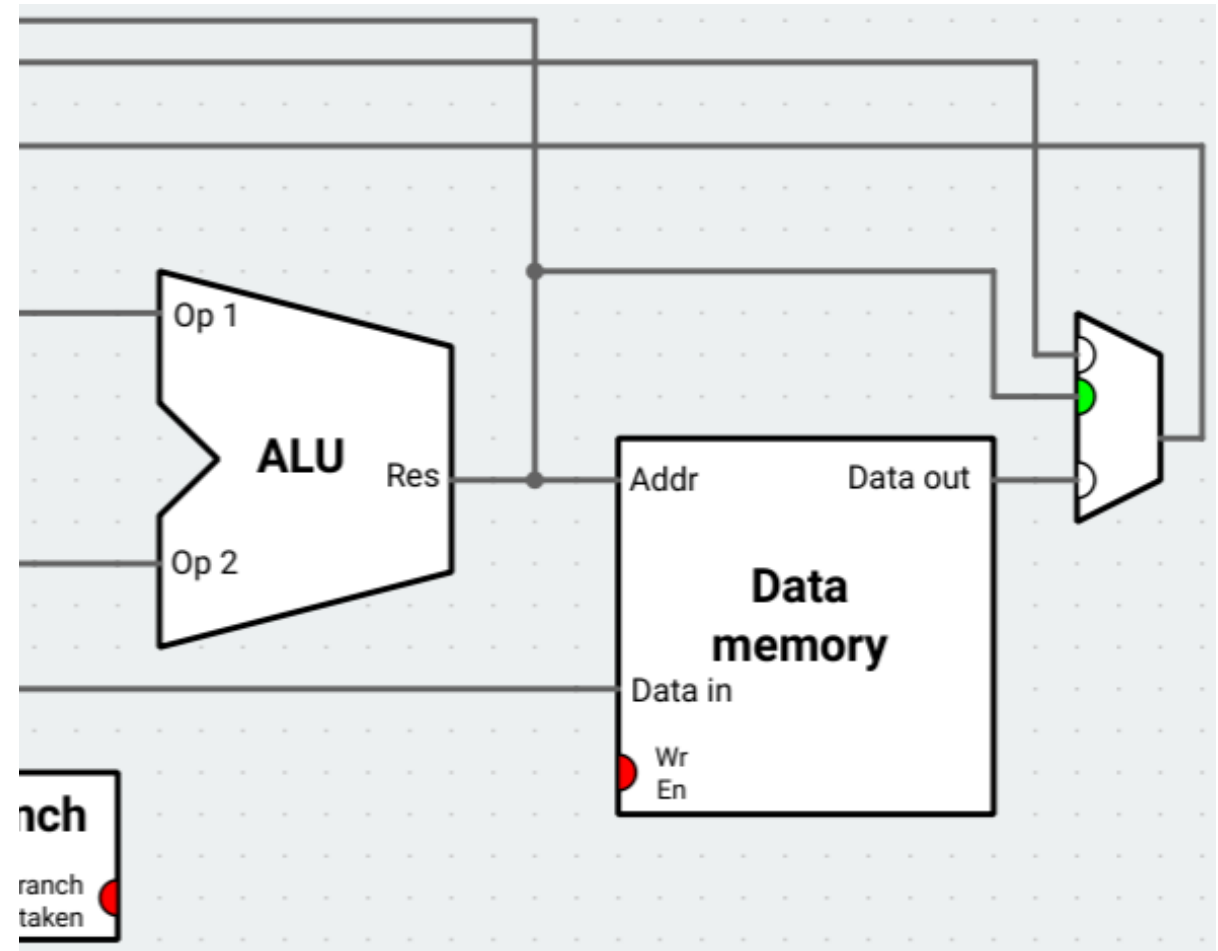
# Memory Stage (MEM)


- Access data memory for load and store instructions
  - Other instructions pass through
- The ALU provides computed memory address ( $rs1+imm$ )
- For stores (sw, sh, sb): the value of rs2 is written to memory at the address
- For loads (lw, lh, lb): the data is read from the address




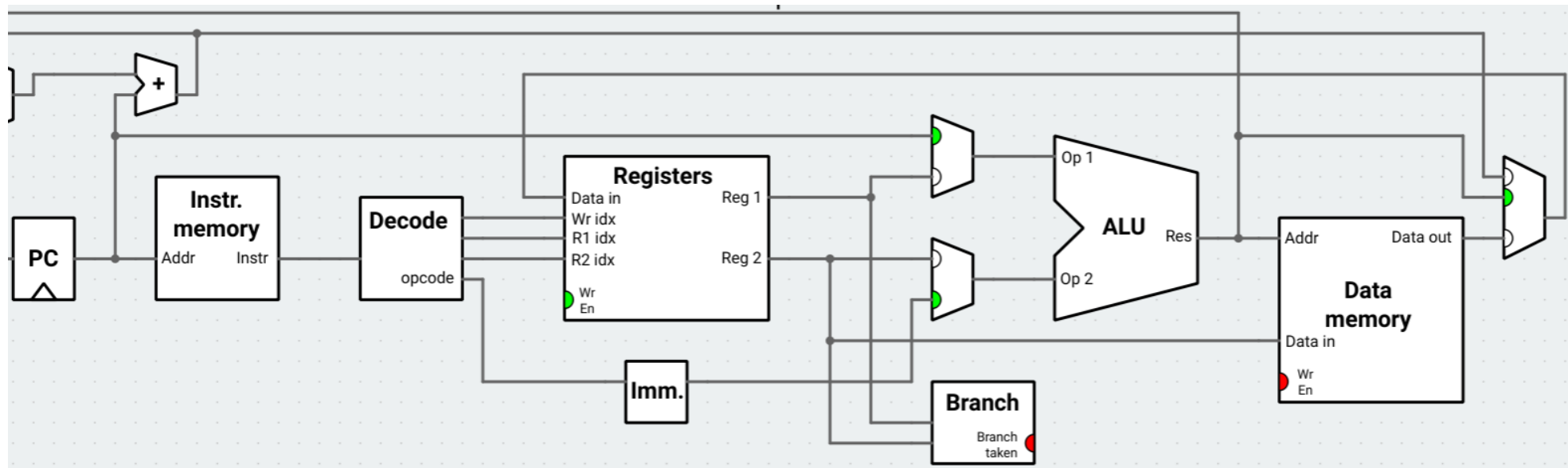
# Write-Back Stage (WB)


- Write the result of the instruction back to the register file
  - ALU Result – for R-type and I-type arithmetic/logic
  - Memory Read Data – for load instructions
  - PC+4 – for jal and jalr (to save the return address)


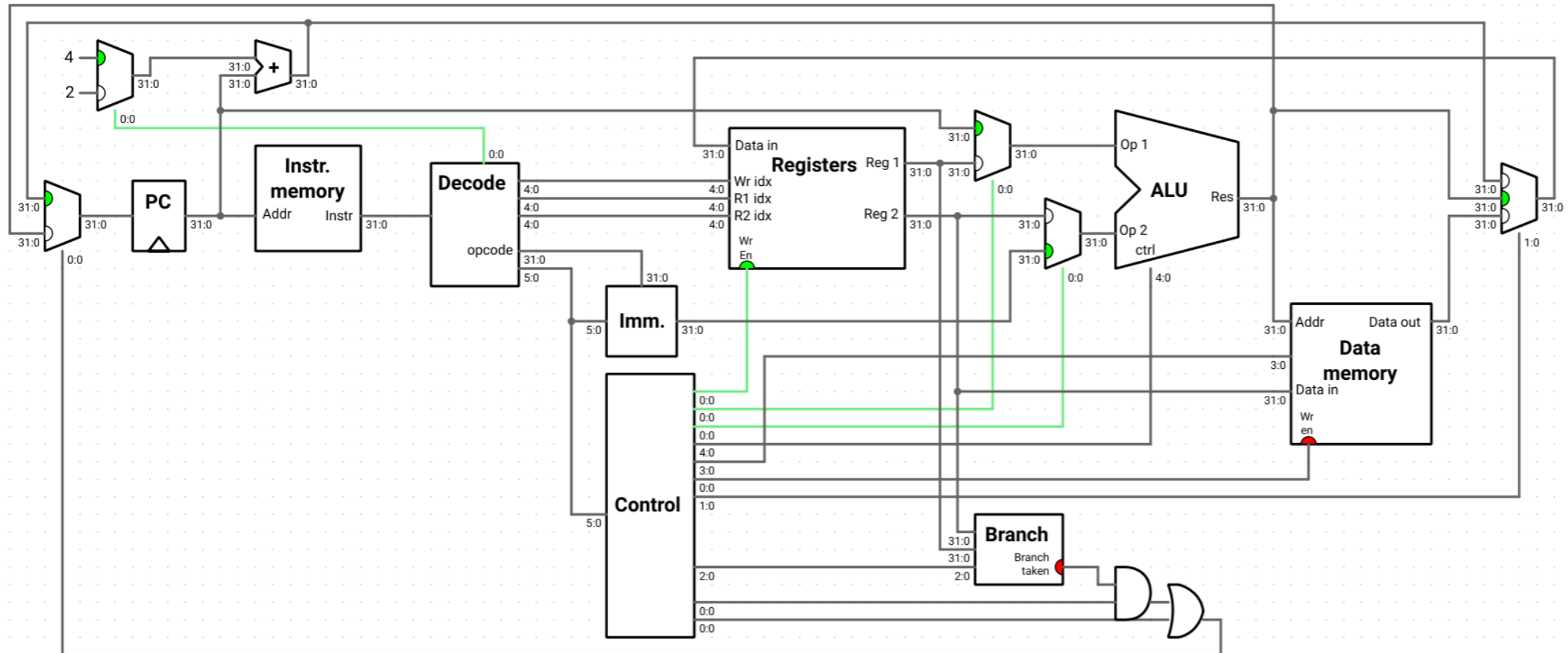
# Control and Datapath



- The Control Unit takes the opcode as primary input and produces all the control signals that steer the datapath



# Stage Computation: R-type (add rd, rs1, rs2)



| Stage      | Action                                                         | Signals / Values                                               |
|------------|----------------------------------------------------------------|----------------------------------------------------------------|
| Fetch      | Read instruction at PC<br>Compute next address                 | $inst \leftarrow IMem[PC]$<br>$PC + 4$                         |
| Decode     | Read registers rs1, rs2                                        | $ReadData1 \leftarrow R[rs1]$<br>$ReadData2 \leftarrow R[rs2]$ |
| Execute    | ALU performs operation <b>OP</b><br>on the two register values | $ALUResult \leftarrow ReadData1 \text{ OP } ReadData2$         |
| Memory     | Nothing                                                        | Pass through                                                   |
| Write Back | Write ALU result to rd                                         | $R[rd] \leftarrow ALUResult$                                   |

# Stage Computation: I-type (addi rd, rs1, imm)



| Stage      | Action                                                  | Signals / Values                                                       |
|------------|---------------------------------------------------------|------------------------------------------------------------------------|
| Fetch      | Read instruction at PC<br>Compute next address          | $inst \leftarrow IMem[PC]$<br>$PC + 4$                                 |
| Decode     | Read registers rs1<br>Generate immediate                | $ReadData1 \leftarrow R[rs1]$<br>$imm \leftarrow SignExt(inst[31:20])$ |
| Execute    | ALU performs operation OP on the register and immediate | $ALUResult \leftarrow ReadData1 \text{ OP } imm$                       |
| Memory     | Nothing                                                 | Pass through                                                           |
| Write Back | Write ALU result to rd                                  | $R[rd] \leftarrow ALUResult$                                           |

# Stage Computation: Load (lw rd, imm(rs1))



| Stage      | Action                                         | Signals / Values                                                       |
|------------|------------------------------------------------|------------------------------------------------------------------------|
| Fetch      | Read instruction at PC<br>Compute next address | $inst \leftarrow IMem[PC]$<br>$PC + 4$                                 |
| Decode     | Read base register rs1<br>Generate immediate   | $ReadData1 \leftarrow R[rs1]$<br>$imm \leftarrow SignExt(inst[31:20])$ |
| Execute    | Compute effective address                      | $ALUResult \leftarrow ReadData1 + imm$                                 |
| Memory     | Read data memory at address                    | $MemData \leftarrow Dmem[ALUResult]$                                   |
| Write Back | Write ALU result to rd                         | $R[rd] \leftarrow MemData$                                             |

- The load instruction exercises **all five stages** meaningfully
- This is the critical-path instruction that determines the minimum clock period in a single-cycle design

# Stage Computation: Store (sw rs2, imm(rs1))



| Stage      | Action                                                                 | Signals / Values                                                                                                    |
|------------|------------------------------------------------------------------------|---------------------------------------------------------------------------------------------------------------------|
| Fetch      | Read instruction at PC<br>Compute next address                         | $inst \leftarrow IMem[PC]$<br>$PC + 4$                                                                              |
| Decode     | Read base register rs1<br>Read data register rs2<br>Generate immediate | $ReadData1 \leftarrow R[rs1]$<br>$ReadData2 \leftarrow R[rs2]$<br>$imm \leftarrow SignExt(inst[31:25], inst[11:7])$ |
| Execute    | Compute effective address                                              | $ALUResult \leftarrow ReadData1 + imm$                                                                              |
| Memory     | Read rs2 value to memory                                               | $Dmem[ALUResult] \leftarrow ReadData2$                                                                              |
| Write Back | Nothing                                                                | No register update                                                                                                  |



# Stage Computation: jalr rd, rs1, offset

| Stage      | Action                                         | Signals / Values                                                       |
|------------|------------------------------------------------|------------------------------------------------------------------------|
| Fetch      | Read instruction at PC<br>Compute next address | $inst \leftarrow IMem[PC]$<br>$PC + 4$                                 |
| Decode     | Read base register rs1<br>Generate immediate   | $ReadData1 \leftarrow R[rs1]$<br>$imm \leftarrow SignExt(inst[31:20])$ |
| Execute    | Compute target address                         | $ALUResult \leftarrow (ReadData1 + imm) \& \sim 1$                     |
| Memory     | Nothing                                        | No register update                                                     |
| Write Back | Save return address in rd                      | $R[rd] \leftarrow PC + 4$                                              |

- The lower bit of the target address is set to 0 to ensure alignment
  - Instructions must start on an even memory address

# Single-Cycle Performance Limitations



- The clock period must accommodate the slowest instruction – lw (uses every stage)
- Example component delays:
  - Instruction Memory: 200 ps
  - Register File Read: 100 ps
  - ALU: 200 ps
  - Data Memory: 200 ps
  - Register File Write: 100 ps
  - Mux and wiring: 50 ps
- Total for lw: 850 ps
- Even though add only needs 650 ps (no data memory access), the clock period must be 850 ps to support lw
  - Every instruction takes one full cycle regardless of complexity
- Also, hardware units sit idle for most of each cycle
- Solution: Pipelining (next lecture)

# Single-Cycle Processor Summary



- **Implementation approach:**

- Express every instruction as a series of simple steps across five stages
- Follow the same general flow for each instruction type
- Assemble registers, memories, and predesigned combinational blocks
- Connect with control logic (muxes selected by the control unit)

- **RISC-V advantages for hardware:**

- Fixed 32-bit instruction length simplifies fetch dramatically
- Regular instruction format (register fields always in the same place) simplifies decode
- Load-store architecture keeps the memory stage clean

- **Limitations of single-cycle design:**

- Clock period determined by slowest instruction (the lw critical path)
- Hardware units active for only a fraction of each cycle
- Too slow to be practical